

Resistors, Inductors and Capacitors




&

**UNIVERSITY
CENTRE**

Resistors

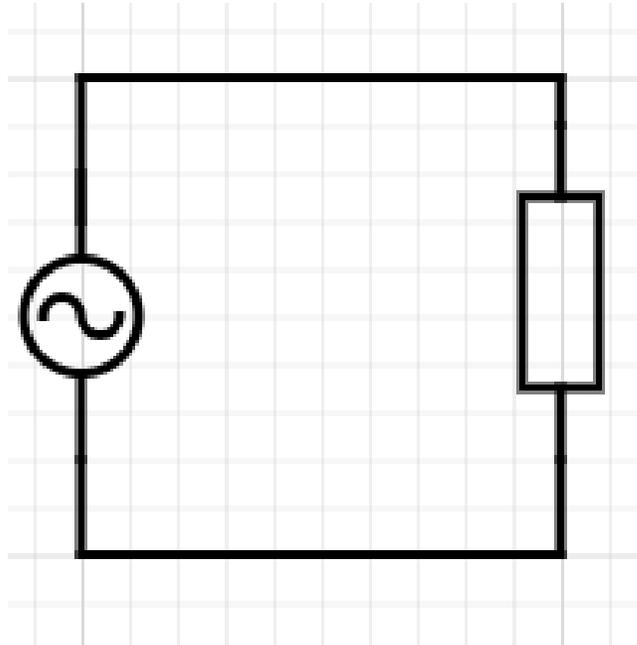- We can use ohms law to work out the value of voltage, current or resistance using ohms law
- But we can only do that for an instantaneous (a fixed point in the t graph)
- Resistors don't cause phase shift as they are a linear component making it easier than other components




$$V = IR \text{ @ instantaneous } t$$
$$V_{\max} = I_{\max} * R$$
$$V_{\text{rms}} = I_{\text{rms}} * R$$


Inductors

- Inductors cause the change in current to slow down (or phase shift)
- In a purely inductive circuit, the voltage will always lead the current by 90°
- In an inductor the relationship between voltage and current can be expressed as:

$$v = L \frac{\Delta i}{\Delta t}$$

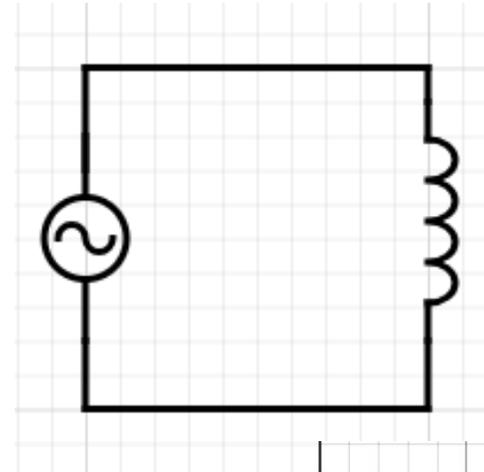

Current
Voltage

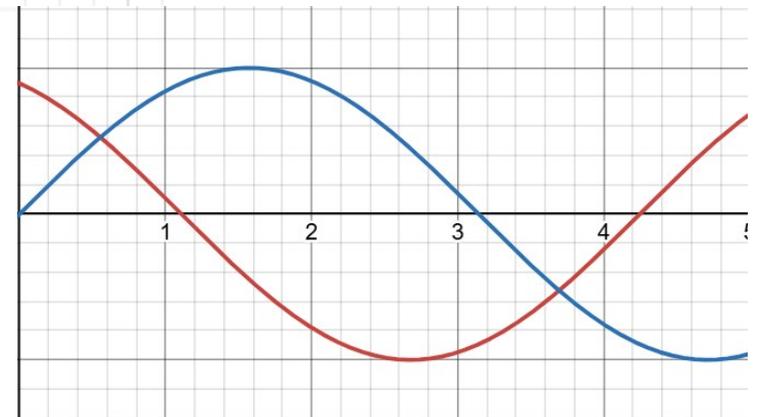


Inductors

- The instantaneous current of a purely inductive circuit is:

$$i = \frac{V_{\max}}{\omega L} \sin(\omega t - 90^\circ)$$

- We can then write ohm's law for inductors as:
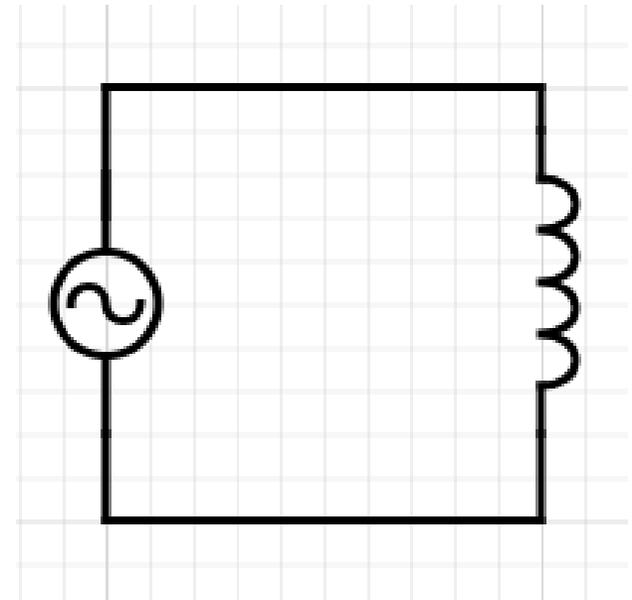
$$I_{\max} = \frac{V_{\max}}{\omega L} \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{\omega L}$$



Inductive Reactance



- Inductive reactance can be thought of as AC resistance
- We can write our inductive reactance as $|X_L|$ which is the magnitude of X_L so just half the vector not thinking about direction
- We can write our ohms version of reactance as $\frac{V}{I} = \omega L @ 90^\circ = j\omega L$ using our imaginary numbers
- $X_L = j\omega L \Omega$

$$\frac{V}{I} = X_L$$

Capacitance

- Capacitors cause the change in voltage to slow down (or phase shift)
- In a purely inductive circuit, the current will always lead the voltage by 90°
- In an inductor the relationship between voltage and current can be expressed as:

$$i = C \frac{\Delta v}{\Delta t}$$

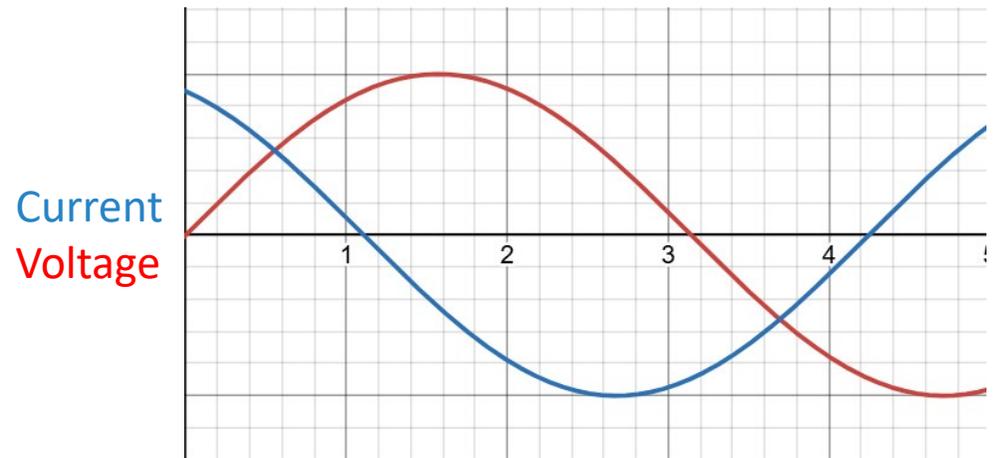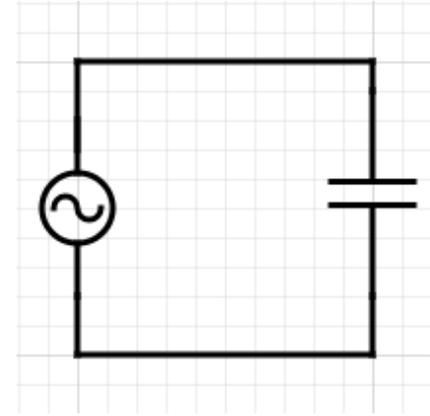


Capacitance

- The instantaneous current of a purely capacitive circuit is:

$$i = \omega C V_{max} \sin(\omega t + 90)$$

- We can then write ohm's law for inductors as:
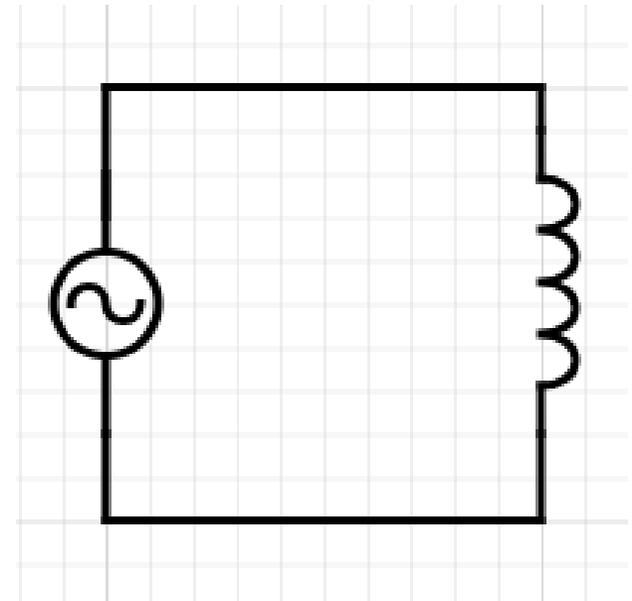
$$i_{max} = \omega C V_{max} \quad i_{rms} = \omega C V_{rms}$$



Inductive Reactance

- Inductive reactance can be thought of as AC resistance
- We can write our inductive reactance as $|X_C|$ which is the magnitude of X_C so just half the vector not thinking about direction
- We can write our ohms version of reactance as $\frac{V}{I} = \frac{1}{\omega C @ 90^\circ} = \frac{1}{j\omega C}$ using our imaginary numbers
- $X_L = \frac{1}{j\omega C} \Omega = -j \frac{1}{\omega C}$

$$\frac{V}{I} = X_C$$