


Advanced Logic Gates



& **UNIVERSITY
CENTRE**


D (Delay) Flip Flop

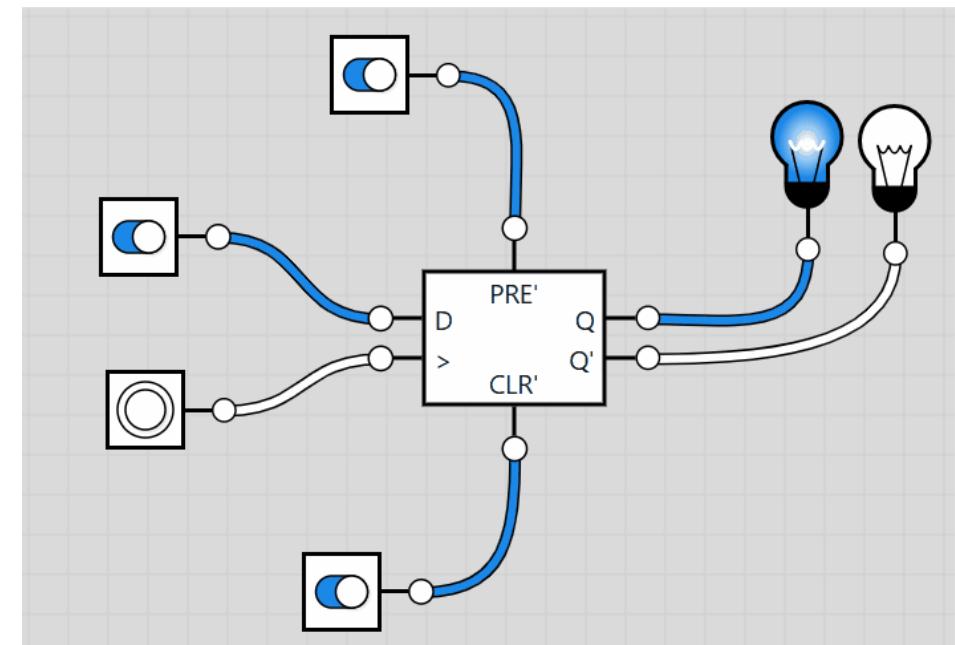- A D Flip Flop is a type of digital memory circuit that captures and stores a single bit of data
 - D is the input into the block
 - > or CLK is the control input, its what determines when the D input is captured
 - Q is the output of the store
 - Q' is the inverted output
 - PRE overwrites the output to be true
 - CLR overwrites the output to be false




T (Toggle) Flip Flop

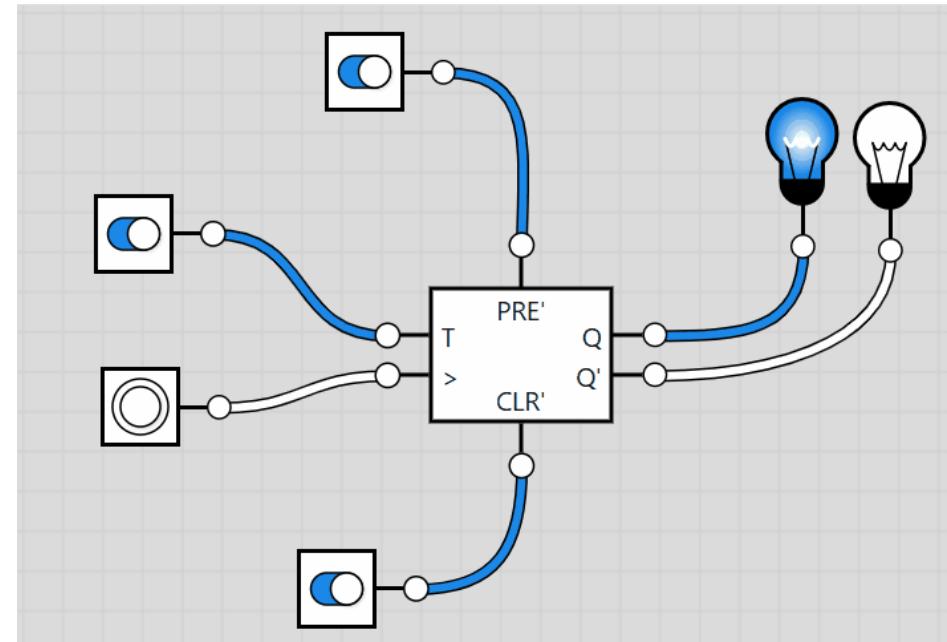- A T Flip Flop is a type of digital memory circuit that captures and stores a single bit of data
 - T is the input of this block 1 means it changes on a clock whereas 0 means it doesn't
 - > or CLK is the control input, it determines when the output flips
 - Q is the output of the store
 - Q' is the inverted output
 - PRE overwrites the output to be true
 - CLR overwrites the output to be false




SR (Set-Reset) Flip Flop

- A SR Flip Flop is a type of digital memory circuit that captures and stores a single bit of data
 - S is the set input so if it's true then the output is true
 - > or CLK is the control input, it determines when the output is set
 - R is the reset input so if it's true then the output will be false
 - Q is the output of the store
 - Q' is the inverted output
- SR Flip Flops have a major disadvantage that when S & R are both true it gives an undefined state which can break circuits

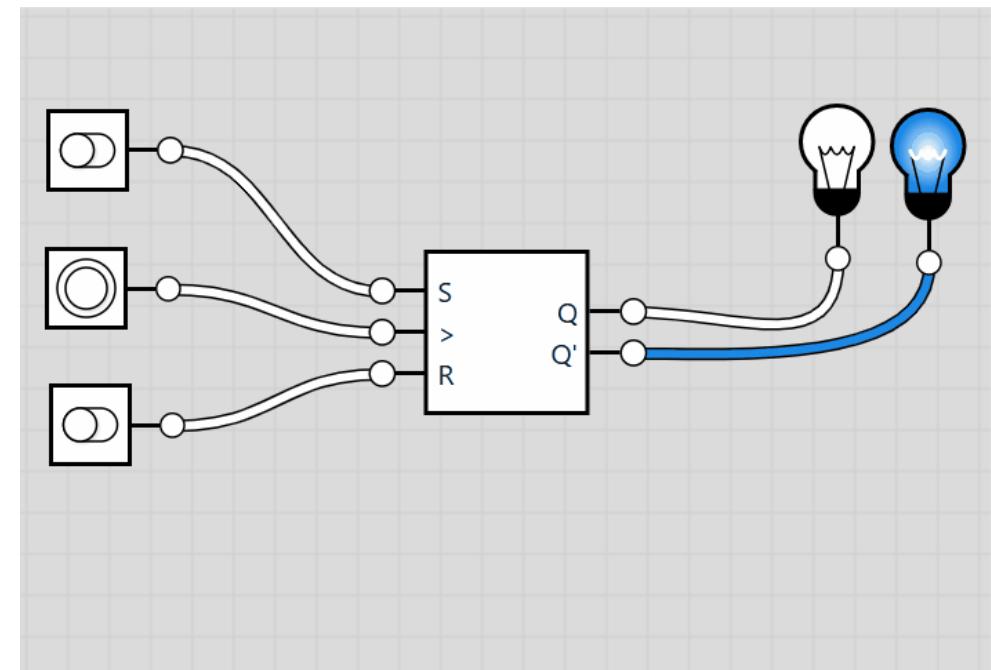

JK Flip Flop

- A JK Flip Flop is a type of digital memory circuit that captures and stores a single bit of data, they work virtually the same as an SR Flip-Flop
 - J is the set input so if it's true then the output is true
 - > or CLK is the control input, it determines when the output is set
 - K is the reset input so if it's true then the output will be false
 - Q is the output of the store
 - Q' is the inverted output
- JK Flip Flops solve the problem of undefined states in an SR Flip Flop by making it so when both inputs are on it becomes a toggle

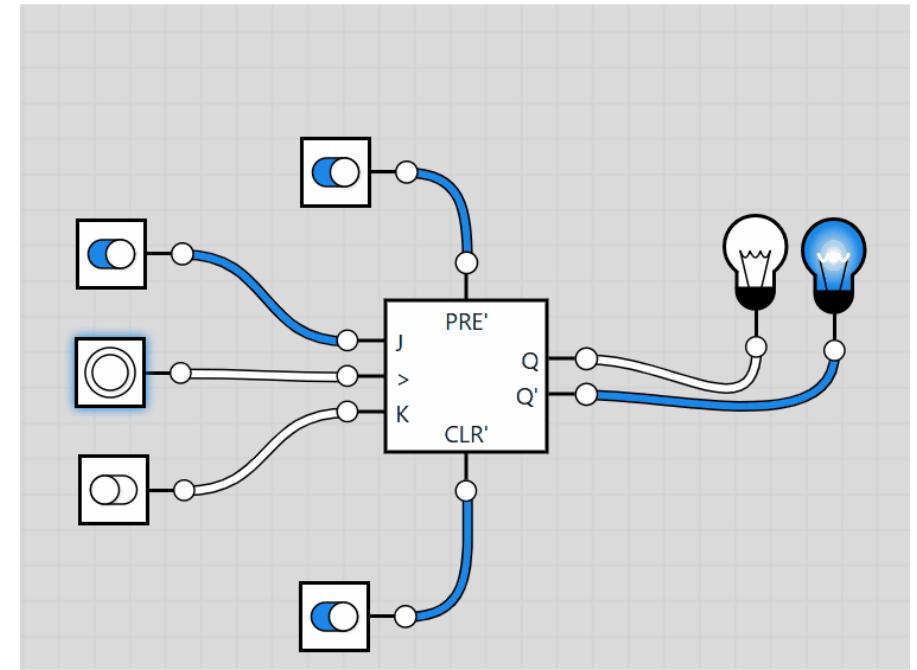

Binary Counter

