

# Kirchoff's Laws



---



& **UNIVERSITY  
CENTRE**
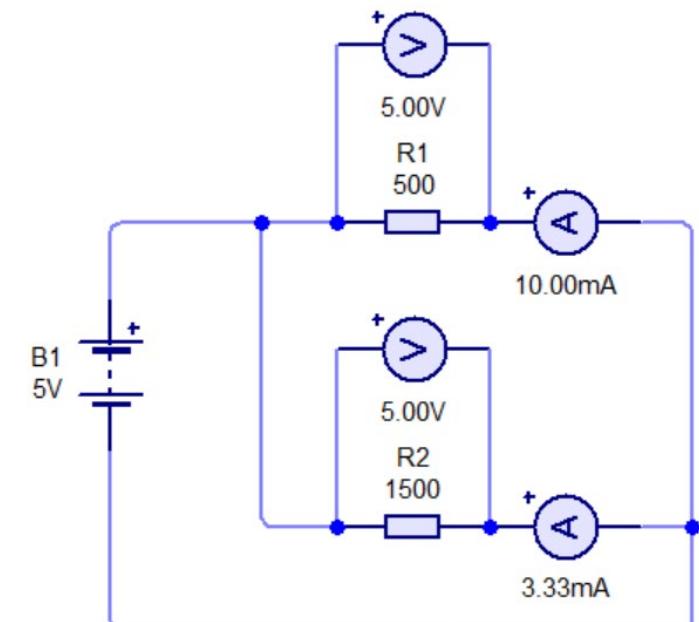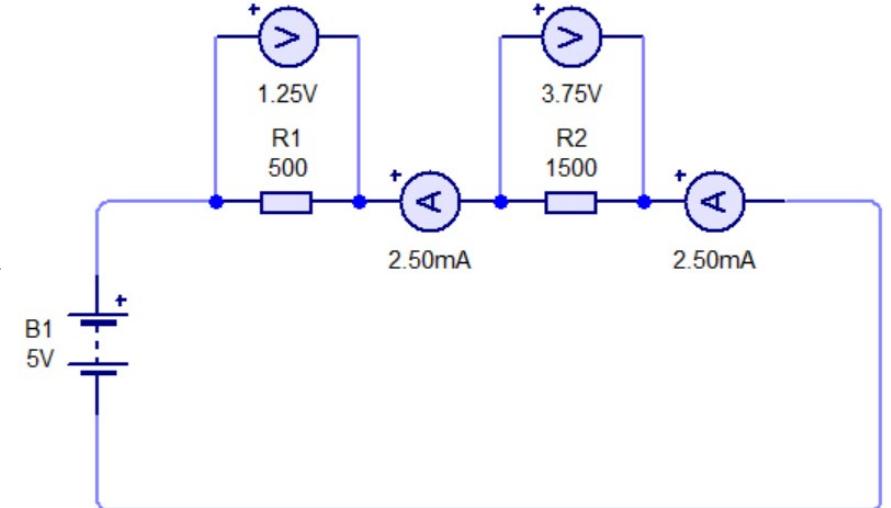
# Recap on DC Circuits


- Ohms law ( $V=IR$ )
- **Series connection:** Current is the same through all components, voltages split
- **Parallel connection:** Voltage is the same across branches, currents split


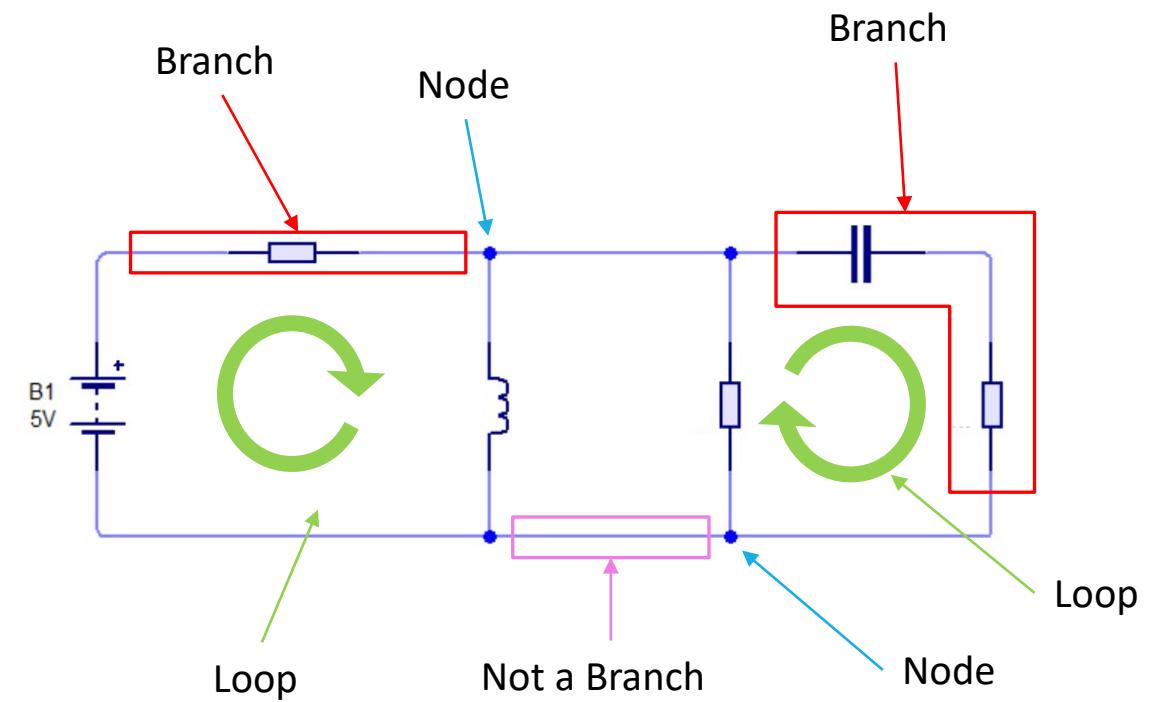
# Parts of DC Circuits

---


- **Node:** A point in a circuit where two or more components are connected.
- **Branch:** A single path connecting two nodes that contains a circuit element (e.g., resistor, voltage source).
- **Loop/Mesh:** Any closed conducting path in a circuit where you can start at one point, travel through elements, and return to the starting point without retracing.


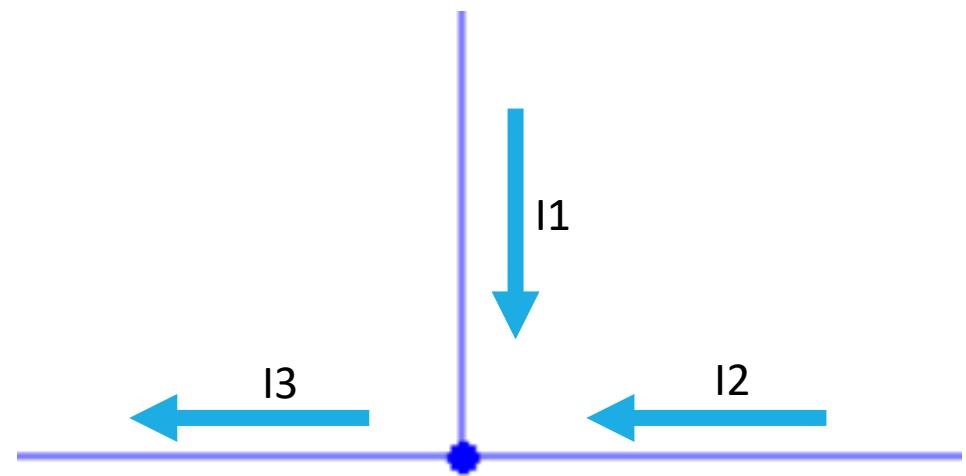
# Kirchoff's Current Law

---


- **Definition:** At any junction, the total current entering = total current leaving
- **Equation form:**  $\sum I_{in} = \sum I_{out}$
- **Basis:** Conservation of charge



$$I_1 + I_2 = I_3$$

# KCL Example

---

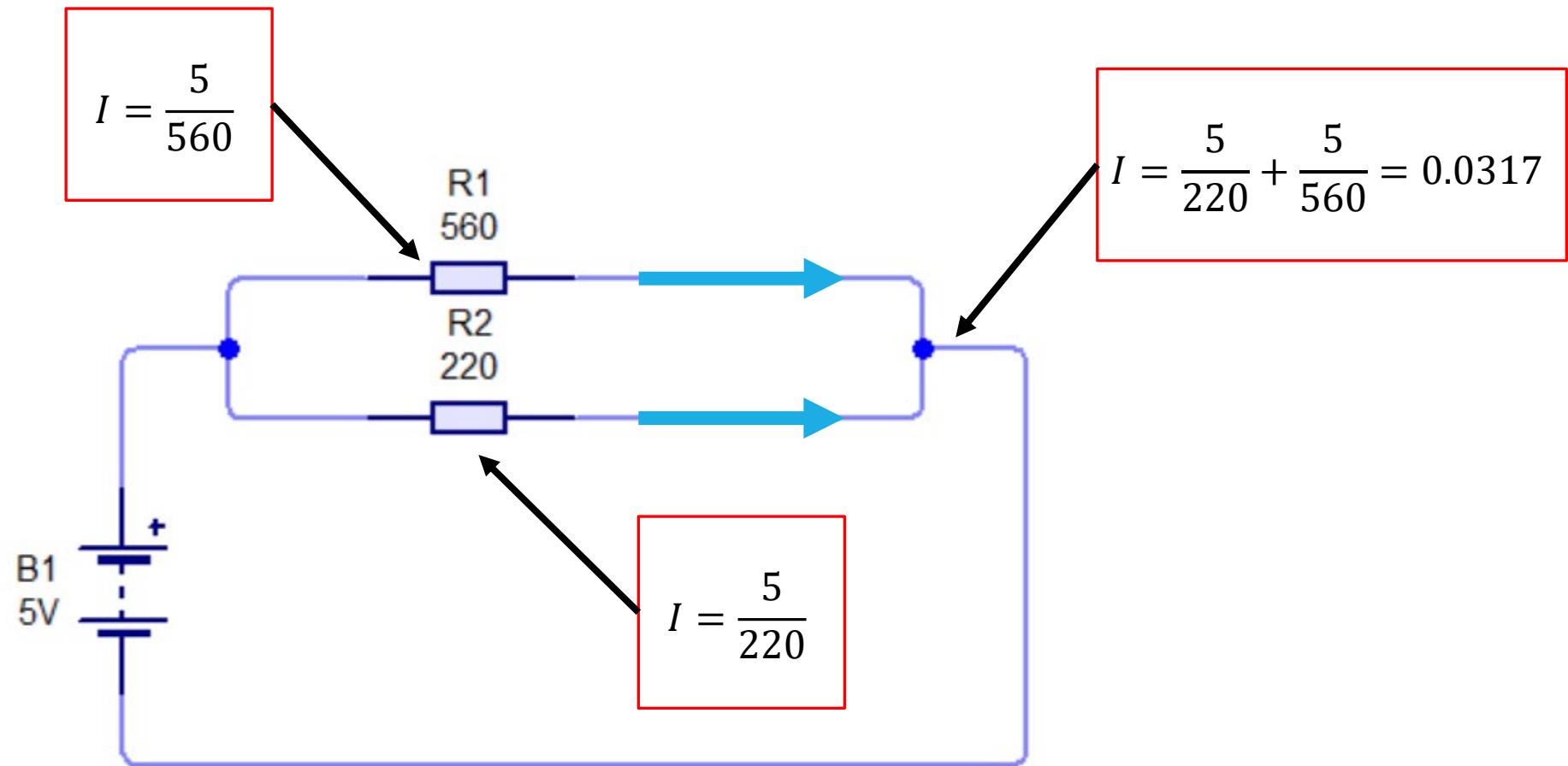


# KCL Example 2

---

- With this example we need to work out the voltage at the node using KCL
- The only thing we must consider is the Voltage at the node in our calculation

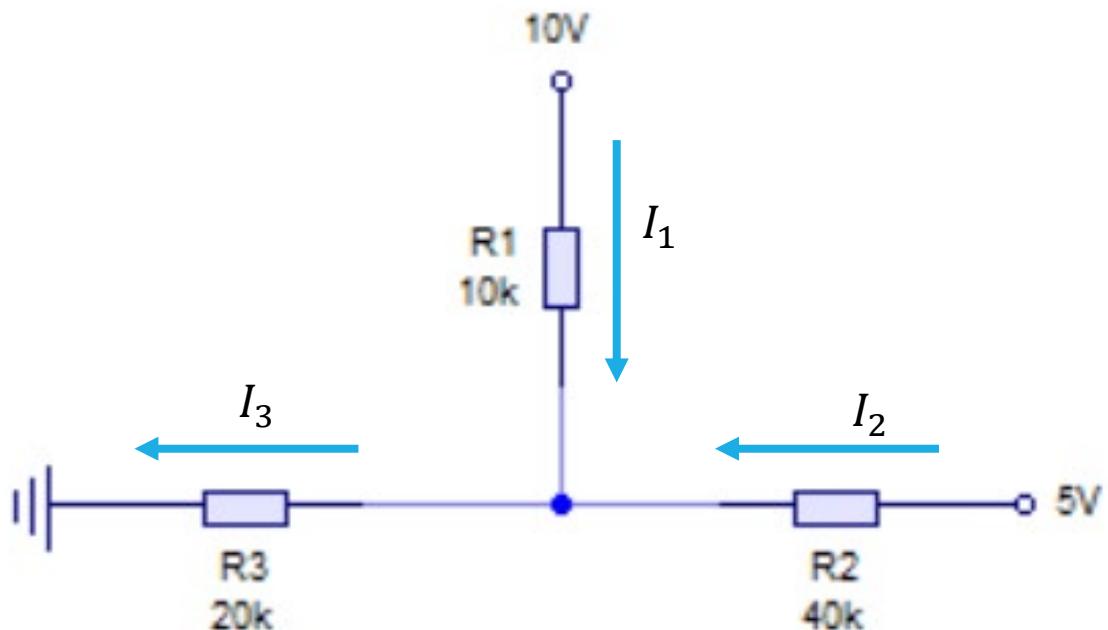
- $$\frac{V_N - V_1}{R_1} + \frac{V_N - V_2}{R_2} + \frac{V_N}{R_3} = 0$$
- $$\frac{V_N - 10}{10000} + \frac{V_N - 5}{40000} + \frac{V_N}{20000} = 0$$


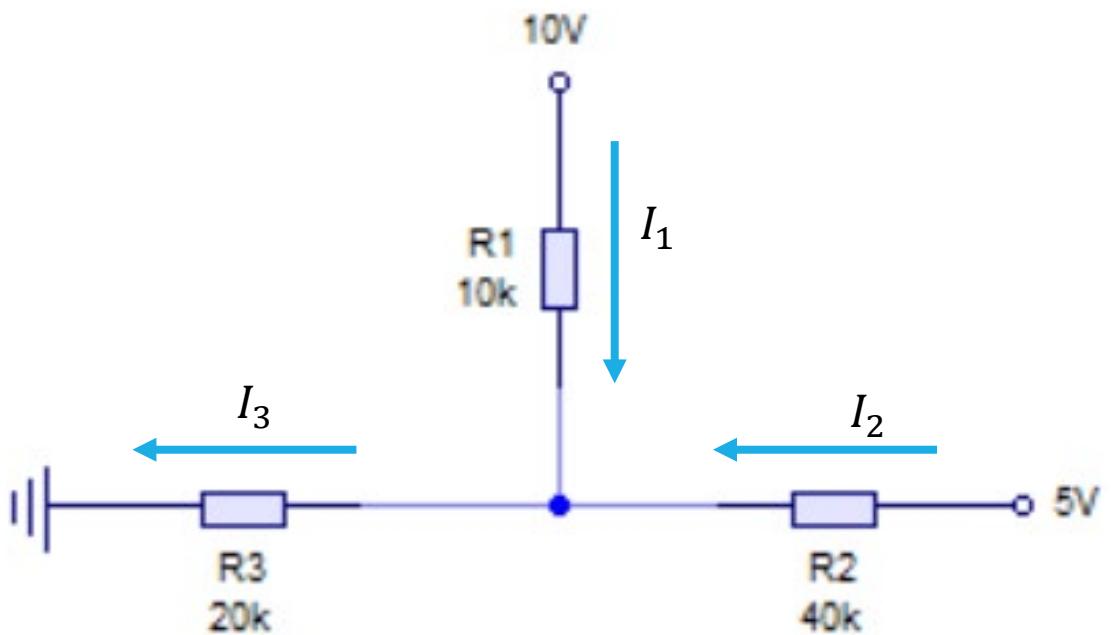
# KCL Example 2


---

- $\frac{V_N - 10}{10000} + \frac{V_N - 5}{40000} + \frac{V_N}{20000} = 0$
- We then clear the denominators by  $\times 40000$
- $4(V_N - 10) + (V_N - 5) + 2(V_N) = 0$
- $4V_N - 40 + V_N - 5 + 2V_N = 0$
- $7V_N - 45 = 0$
- $V_N = 6.428571429$


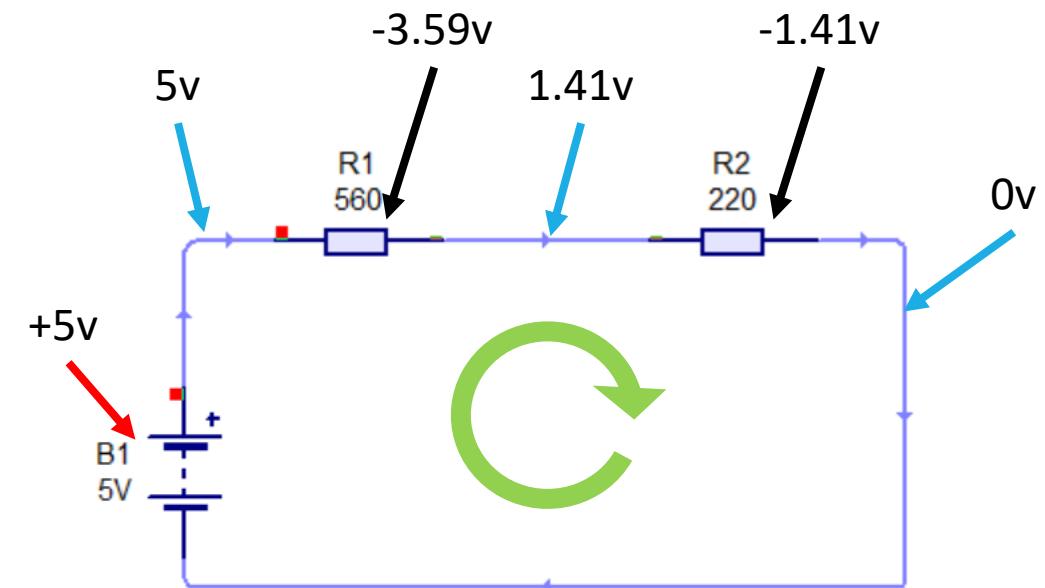
# Kirchoff's Voltage Law

- **Definition:** The sum of all voltages around any closed loop in a circuit is zero.
- **Equation form:**  $\sum V = 0$
- **Meaning:** Energy is conserved—voltage rises (sources) are balanced by voltage drops (loads).
- **Rule of thumb:** When you go around a loop, add rises as positive, drops as negative.




$$5v - 3.59v - 1.41v = 0v$$

# KVL Example

---

$$V_1 = 1.25 * 3 = 3.75$$

$$V_2 = 1.25 * 1 = 1.25$$

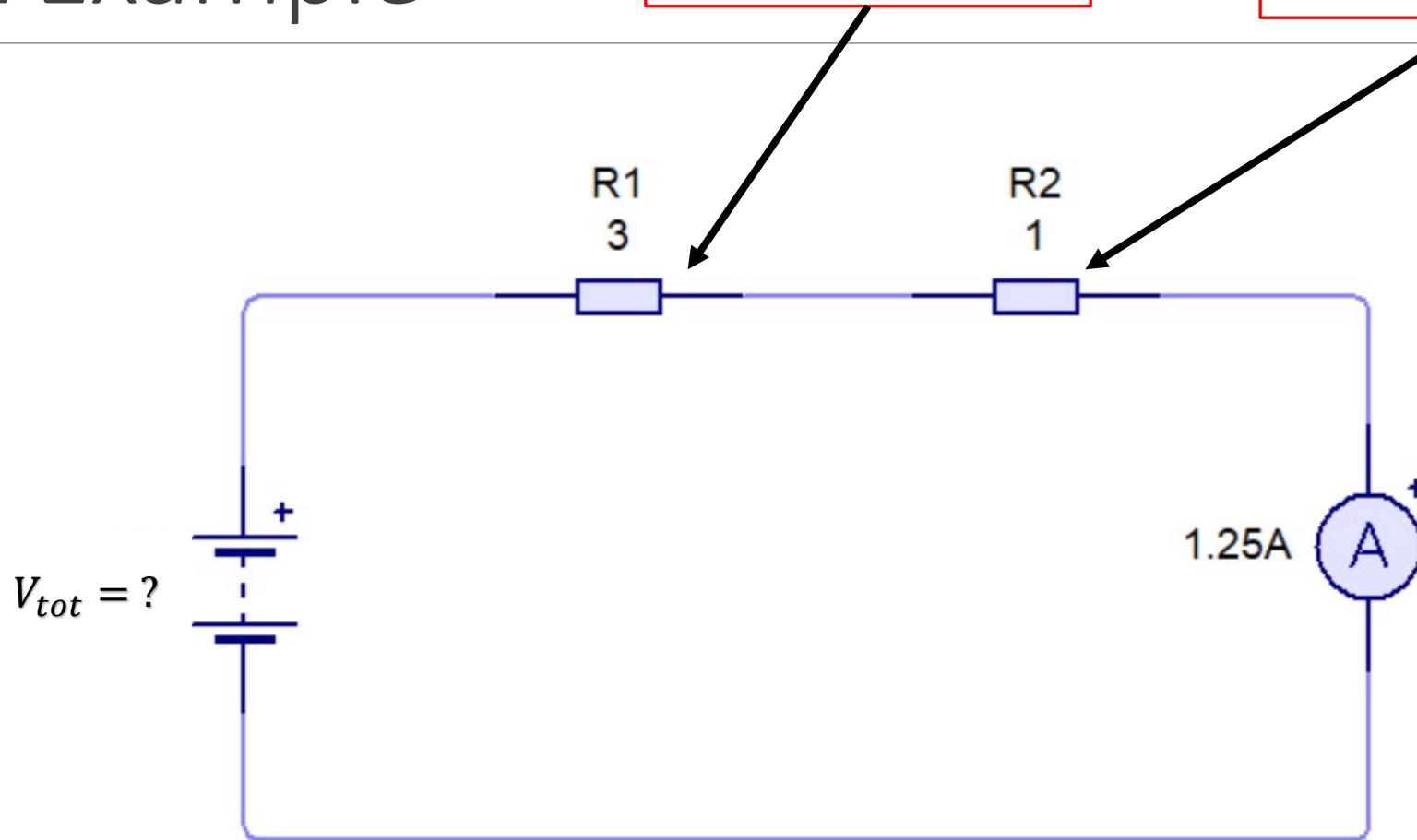


# KVL Example

$$V_{tot} = V_1 + V_2 = 3.75 + 1.25 = 5$$

$$V_1 = 1.25 * 3 = 3.75$$

$$V_2 = 1.25 * 1 = 1.25$$

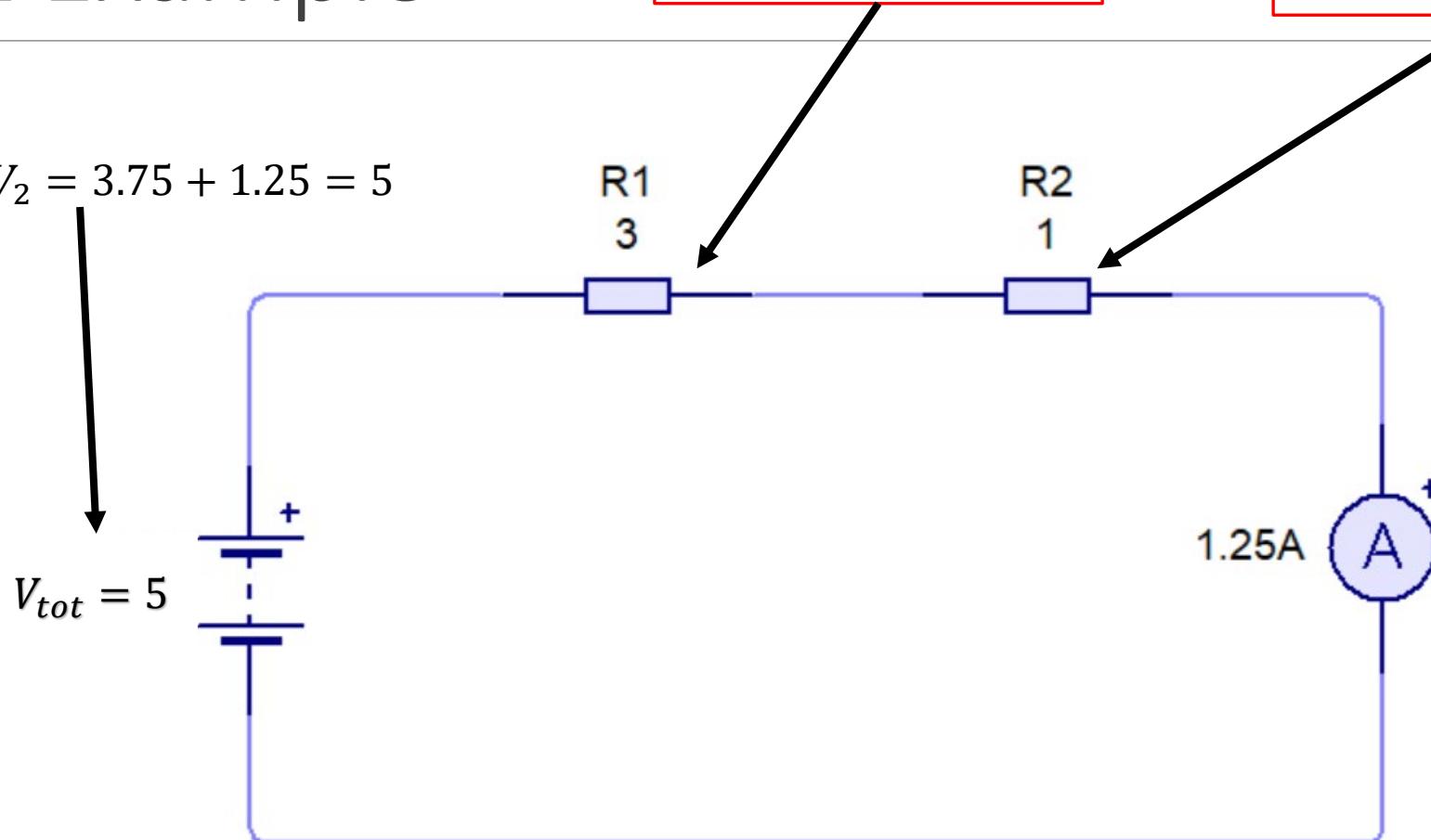

# Mesh/Loop Analysis

- We mainly use Kirchoff's Laws in Mesh Analysis
- Mesh Analysis allows us to look at voltage and current values all around the circuit
- We do this by dividing our circuit into “meshes” or loops and then doing KCL and KVL analysis

