

# Mesh Analysis

---




& **UNIVERSITY  
CENTRE**
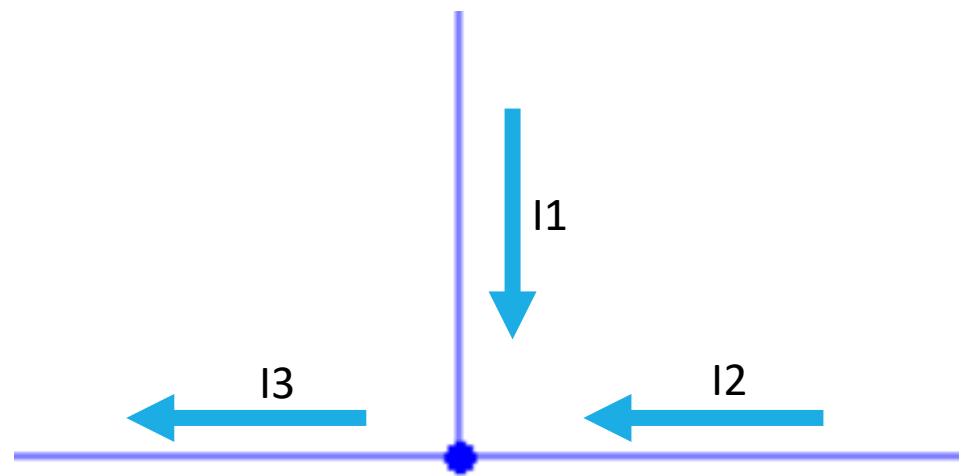
# Kirchoff's Current Law

---


- **Definition:** At any junction, the total current entering = total current leaving
- **Equation form:**  $\sum I_{in} = \sum I_{out}$
- **Basis:** Conservation of charge



$$I_1 + I_2 = I_3$$
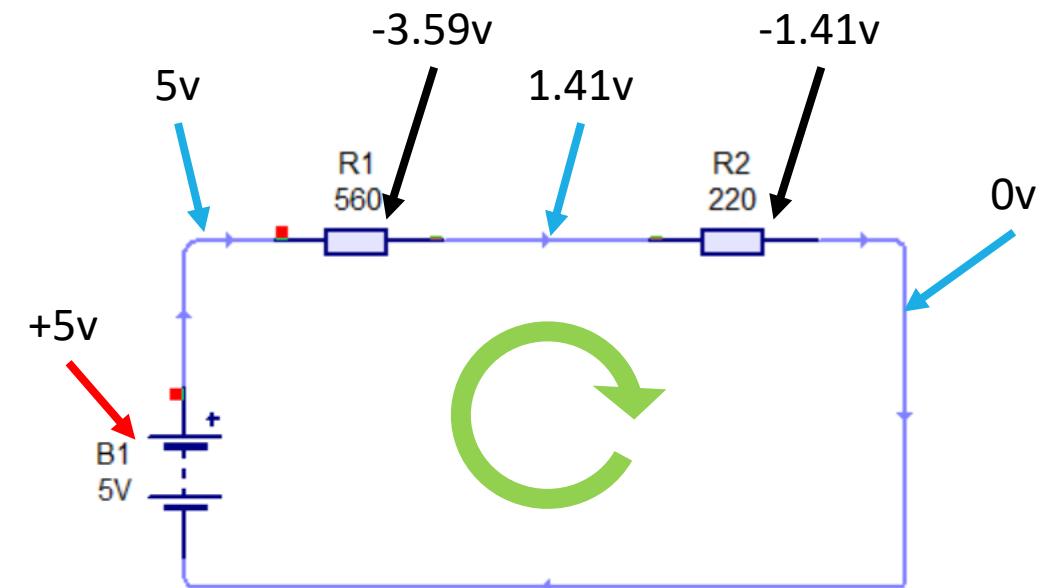
# Kirchoff's Voltage Law

- **Definition:** The sum of all voltages around any closed loop in a circuit is zero.
- **Equation form:**  $\sum V = 0$
- **Meaning:** Energy is conserved—voltage rises (sources) are balanced by voltage drops (loads).
- **Rule of thumb:** When you go around a loop, add rises as positive, drops as negative.




$$5v - 3.59v - 1.41v = 0v$$
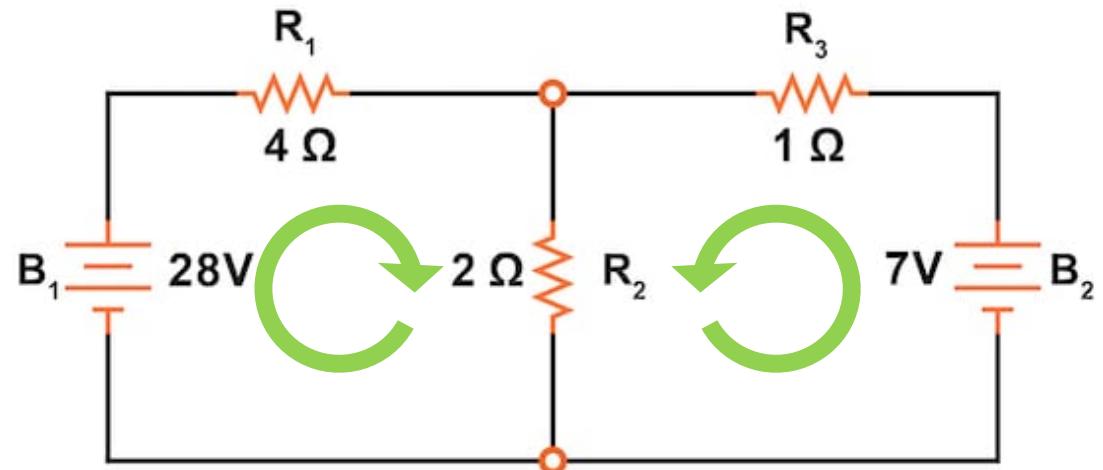
# Let's Solve this together

---


- We can calculate the current and voltage drop across every part of this
- Our first step is to split our circuit into loops
- We usually put the direction for our loops based on the sources in it


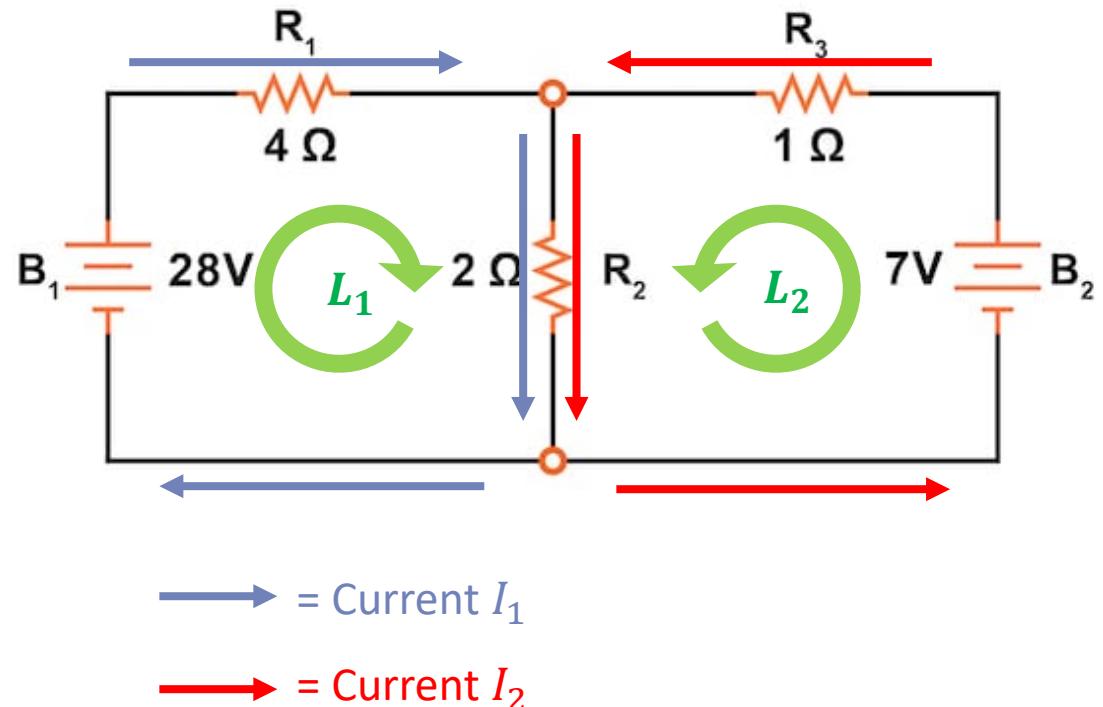
# Let's Solve this together

---


- Each of these loops has their own current, so we can assign a current to each loop:
  - $L_1$  has  $I_1$  in the loop
  - $L_2$  has  $I_2$  in the loop
- We can draw on our circuit the current flows
- We know where both loops interact, we must add the current according to KCL
- This means:
  - $R_1$  has  $I_1$  going through it
  - $R_3$  has  $I_2$  going through it
  - $R_2$  has  $I_1 + I_2$  going through it


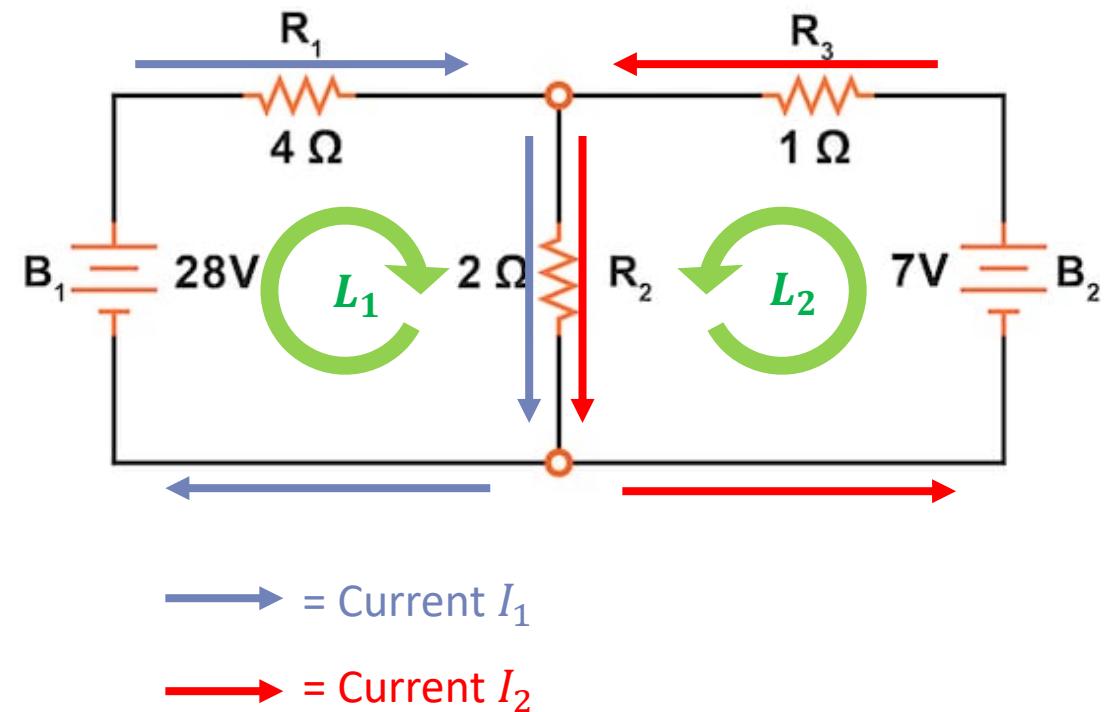
# Let's Solve this together

---


- Based on Kirchoff's Voltage Law we know that the voltage drop across all the components in a loop must equal the voltage we put in
- We also know that  $V = IR$
- Therefore, we can make an equation for the voltage drop across both loops


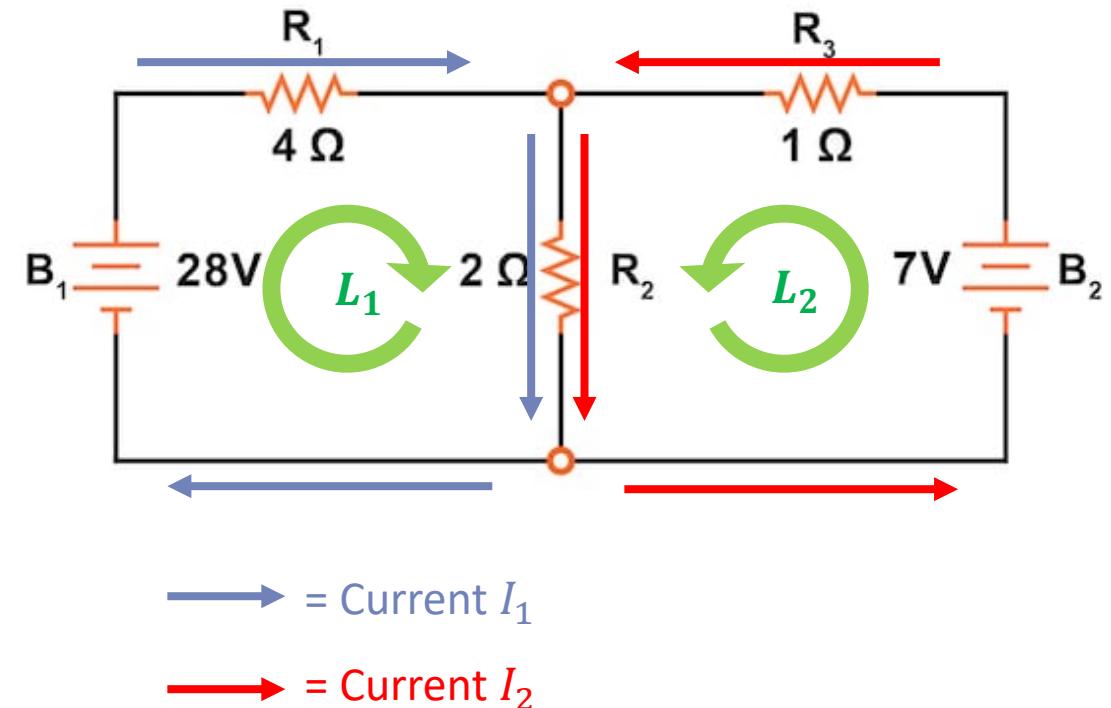
# Let's Solve this together

---


- For Loop L1:
- We have a 28v source, and 2 resistors in the loop
- So we can write this for the loop:
- $\sum V_{source} = \sum V_{drop}$
- $B_1 = I_1 R_1 + (I_1 + I_2) R_2$
- $28 = 4I_1 + 2(I_1 + I_2)$


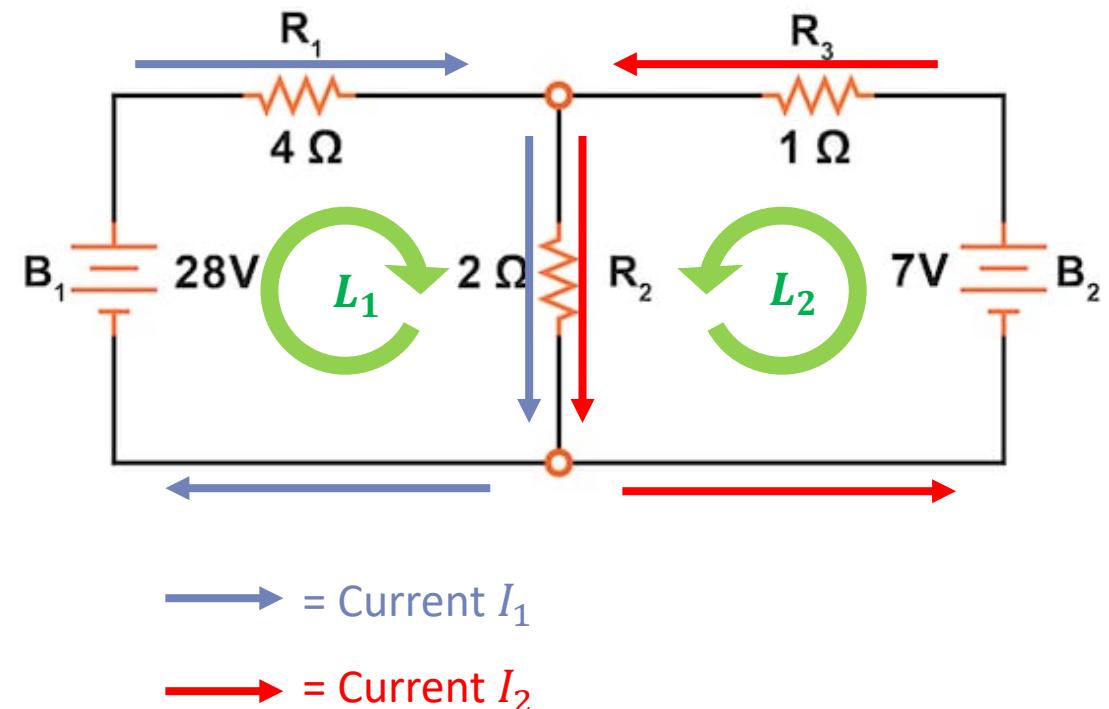
# Let's Solve this together

---


- For Loop L2:
- We have a 7v source, and 2 resistors in the loop
- So we can write this for the loop:
- $\sum V_{source} = \sum V_{drop}$
- $B_2 = I_2 R_3 + (I_1 + I_2) R_2$
- $7 = 1I_2 + 2(I_1 + I_2)$


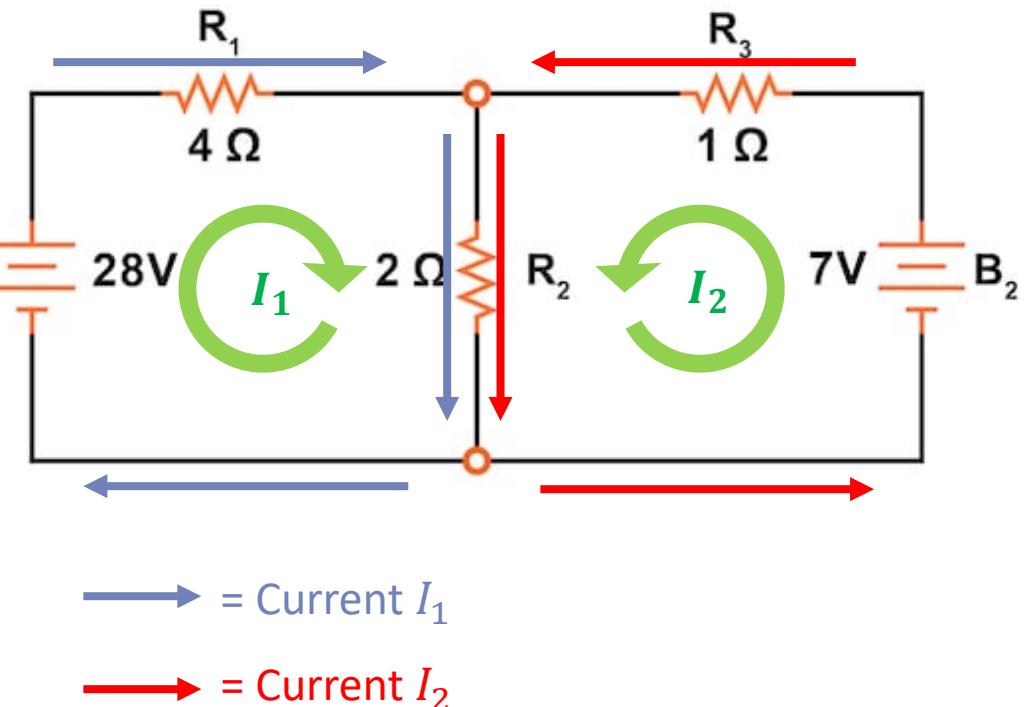
# Let's Solve this together

---


- $L_1: 28 = 4I_1 + 2(I_1 + I_2)$
- $L_2: 7 = 1I_2 + 2(I_1 + I_2)$
- This leaves us two simultaneous equations meaning we can then work out  $I_1$  and  $I_2$
- You can solve these how you like but for this example I'm using substitution


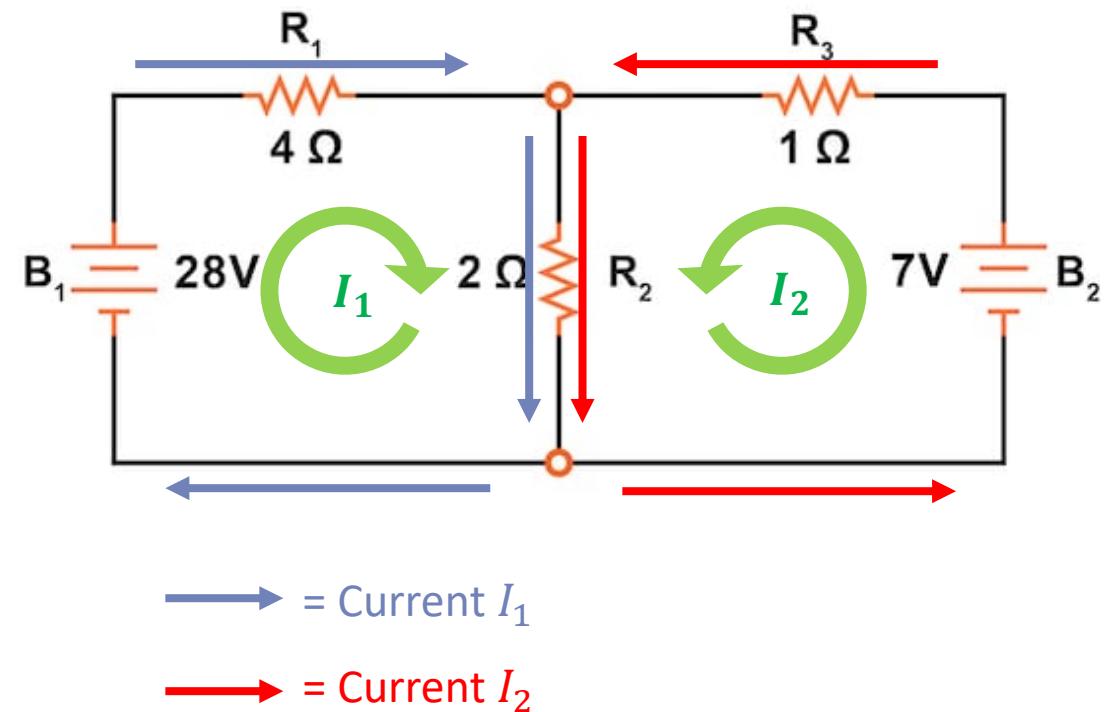
# Let's Solve this together

---


- We start by rearranging  $L_1$  to give us one of the current values (either  $I_1$  or  $I_2$ )
- $L_1: 28 = 4I_1 + 2(I_1 + I_2)$
- We can expand out our brackets and then combine like terms
- $L_1: 28 = 4I_1 + 2I_1 + 2I_2$
- $L_1: 28 = 6I_1 + 2I_2$


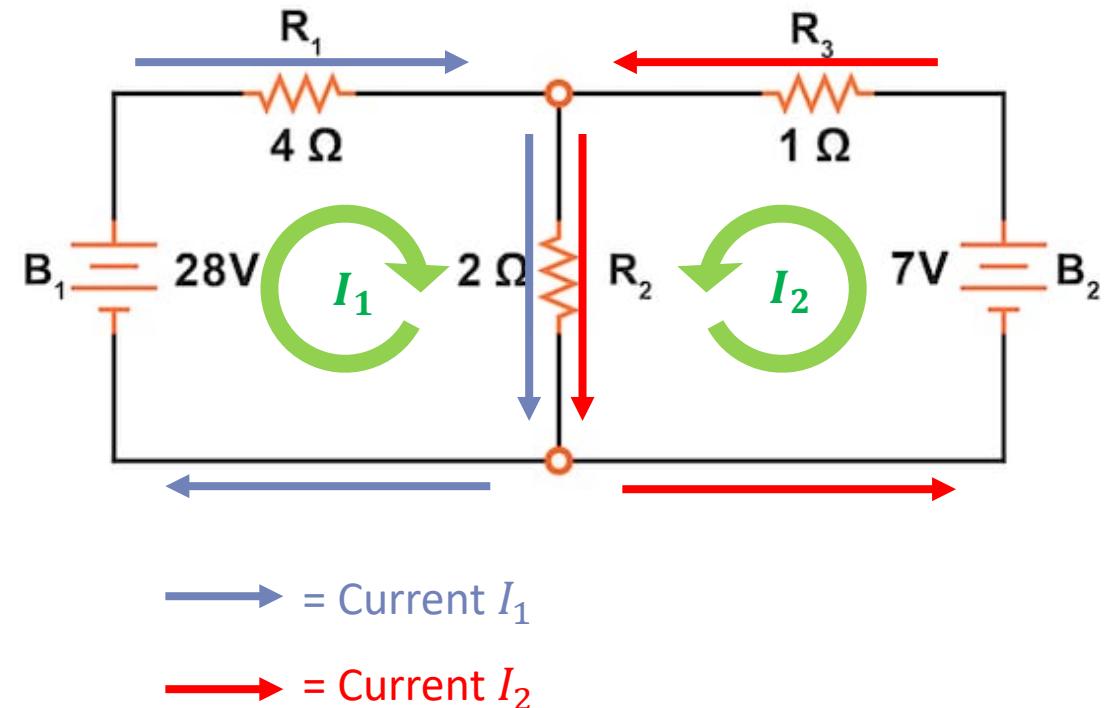
# Let's Solve this together

---


- $L_1: 28 = 6I_1 + 2I_2$
- Let's make this all equal to  $I_1$ :
- $L_1: 28 - 2I_2 = 6I_1$
- $L_1: \frac{28 - 2I_2}{6} = I_1$
- We can now plug this into  $L_2$


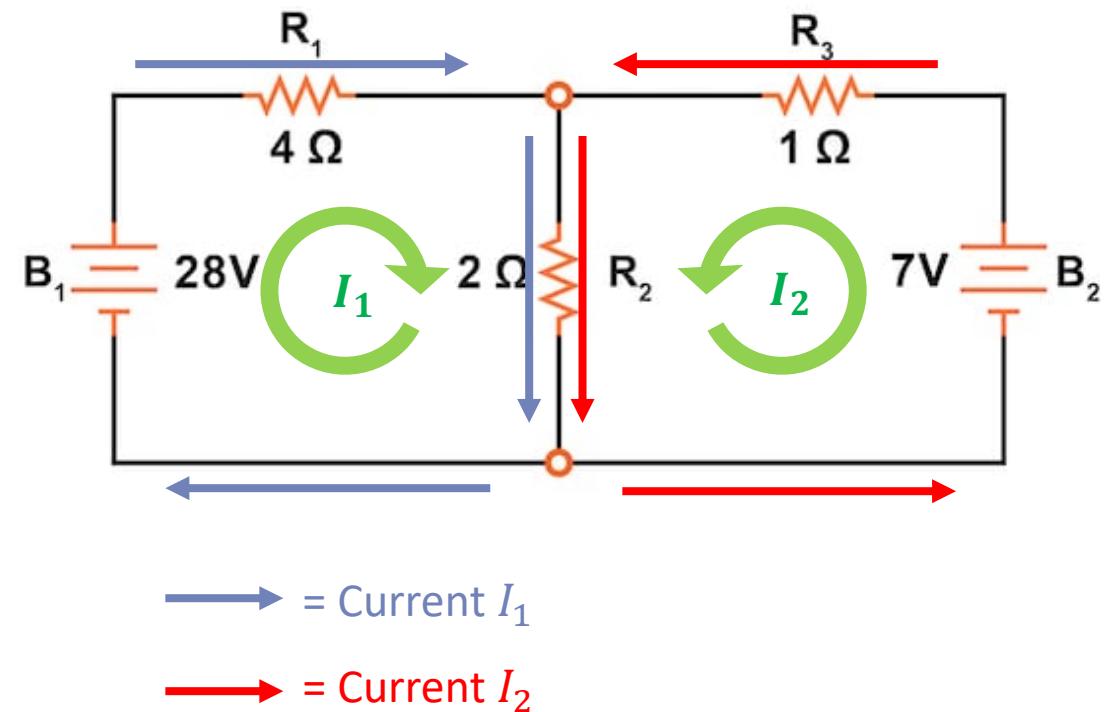
# Let's Solve this together

---


- $L_1: \frac{28-2I_2}{6} = I_1$
- $L_2: 7 = 1I_2 + 2(I_1 + I_2)$
- First let's expand the brackets again and collect like terms
- $L_2: 7 = 1I_2 + 2I_1 + 2I_2$
- $L_2: 7 = 2I_1 + 3I_2$


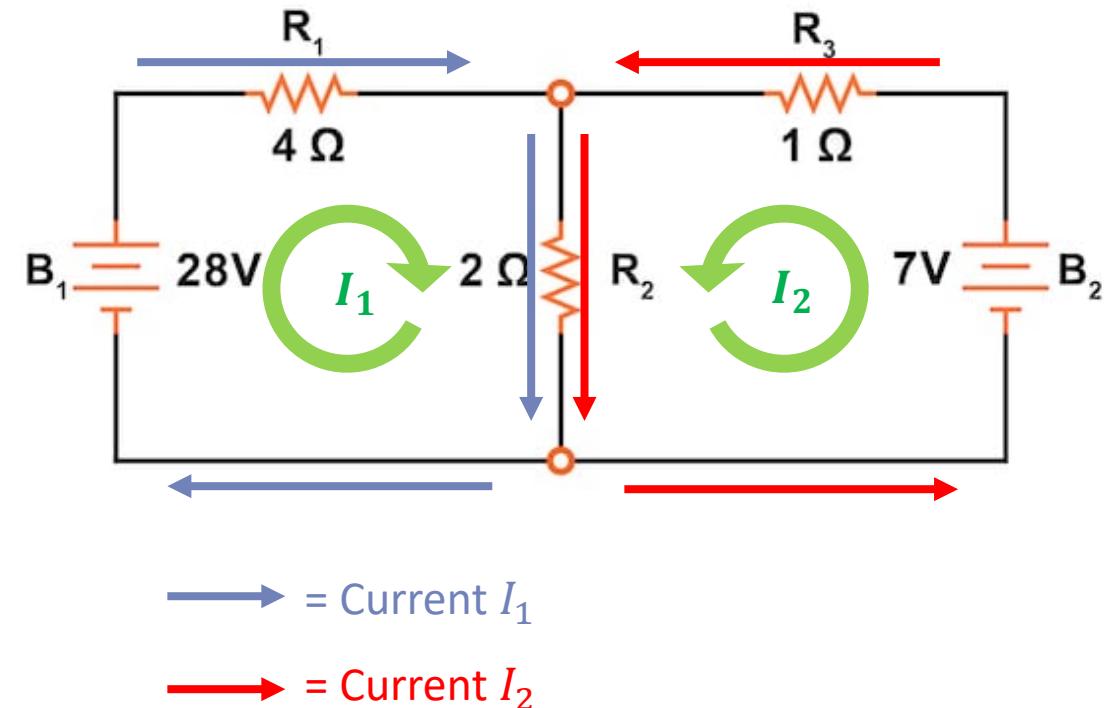
# Let's Solve this together

---


- $L_1: \frac{28-2I_2}{6} = I_1$
- $L_2: 7 = 3I_2 + 2I_1$
- Let's plug it in
- $L_2: 7 = 3I_2 + 2\left(\frac{28-2I_2}{6}\right)$
- Then let's expand the brackets
- $L_2: 7 = 3I_2 + \frac{56-4I_2}{6}$


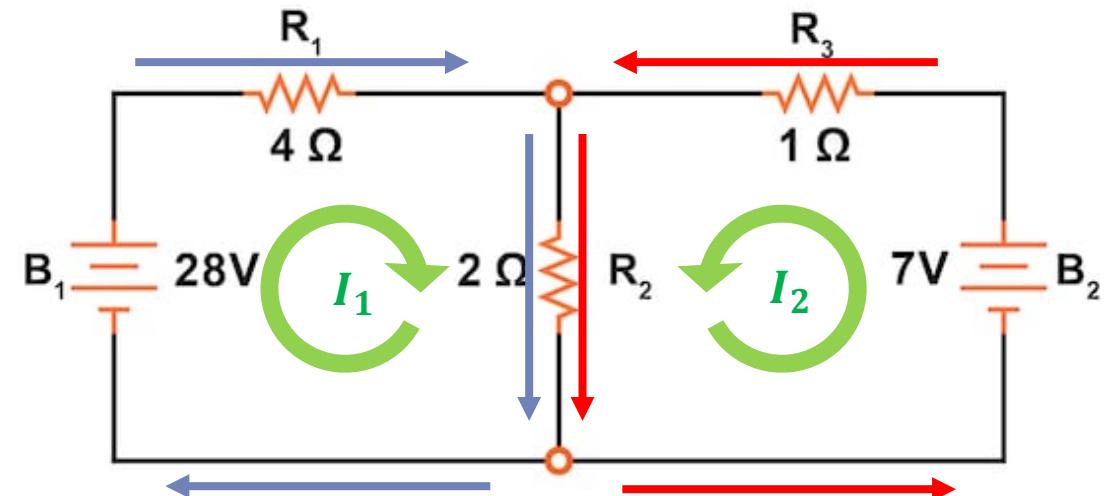
# Let's Solve this together

---

- $L_2: 7 = 3I_2 + \frac{56 - 4I_2}{6}$
- Let's get  $I_2$  by itself by rearranging the equation
- $42 = 18I_2 + 56 - 4I_2$
- $-14 = 14I_2$
- $I_2 = -1A$
- Having a negative current is fine, it just means its flowing the opposite way



→ = Current  $I_1$

→ = Current  $I_2$

# Let's Solve this together

---

- $I_2 = -1A$
- We can plug this value back into the other equation we have
- $\frac{28-2(-1)}{6} = I_1$
- $\frac{30}{6} = I_1$
- $I_1 = 5A$

