

# AC Circuit Analysis

---



UNIVERSITY  
CENTRE

# Circuit with Resistors

---

- We know resistors don't change the phase of the voltage or current.
- We can just use these equations to work out the values in a resistive circuit
  - Voltage = Current \* Resistance
  - Power = Voltage \* Current



$$V = I * R$$

$$120 = I * 100$$

$$I = 1.2A$$

$$P = V * I$$

$$P = 120 * 1.2$$

$$P = 144W$$

# Circuits with Inductors

---

- For circuits with inductors, we have a phase shift
- This means we need to change our equations:
  - Inductive Reactance =  $2\pi * \text{Frequency} * \text{Reactance}$
  - Voltage = Current \* Inductive Reactance



$$\begin{aligned}X_L &= 2\pi f L \\X_L &= 2\pi * 1000 * 5 \\X_L &= 31415.92654\end{aligned}$$

$$\begin{aligned}V &= IX_L \\120 &= I * 3141592654 \\I &= 0.003819718634\end{aligned}$$

# Circuits with Capacitors

---

- For circuits with capacitors, we again have a phase shift
- This means we need to use the equations:
  - Capacitive Reactance =  $1/2\pi \times \text{frequency} \times \text{capacitance}$
  - Voltage = Current \* Capacitive Reactance



$$X_C = \frac{1}{2\pi f C}$$




$$X_C = \frac{1}{2\pi * 1000 * 5}$$
$$X_C = 3.18309886 * 10^{-5}$$

$$V = IX_C$$
$$120 = I * 3.18309886 * 10^{-5}$$
$$I = 3769911.184$$
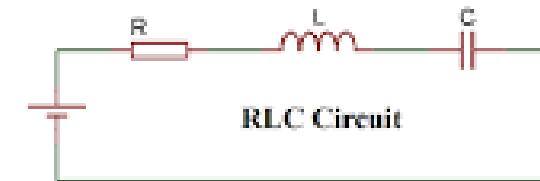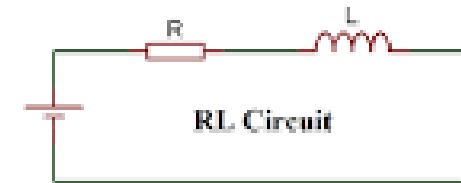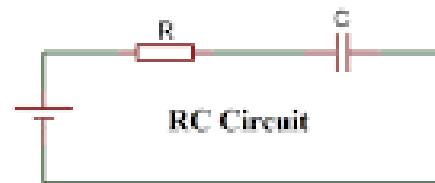
# RLC, RC and RL Circuits

---

- RLC Circuits contain all 3 components;
  - A Resistor (R)
  - An Inductor (L)
  - A Capacitor (C)
- RL Circuits contain two of the components;
  - A Resistor (R)
  - An Inductor (L)
- RC Circuits contain two of the components;
  - A Resistor (R)
  - A Capacitor (C)



# Series RL, RC and RLC Circuits


---

- For each of the different series circuits you can use impedance to work out voltage and current using the equation:
  - $Z = \sqrt{R^2 + (X_L - X_C)^2}$  where:
    - Z = Impedance
    - R = Resistance
    - $X_L$  = Inductive Reactance
    - $X_C$  = Capacitive Reactance
  - Note when you don't have an inductor or a capacitor you just set them to 0
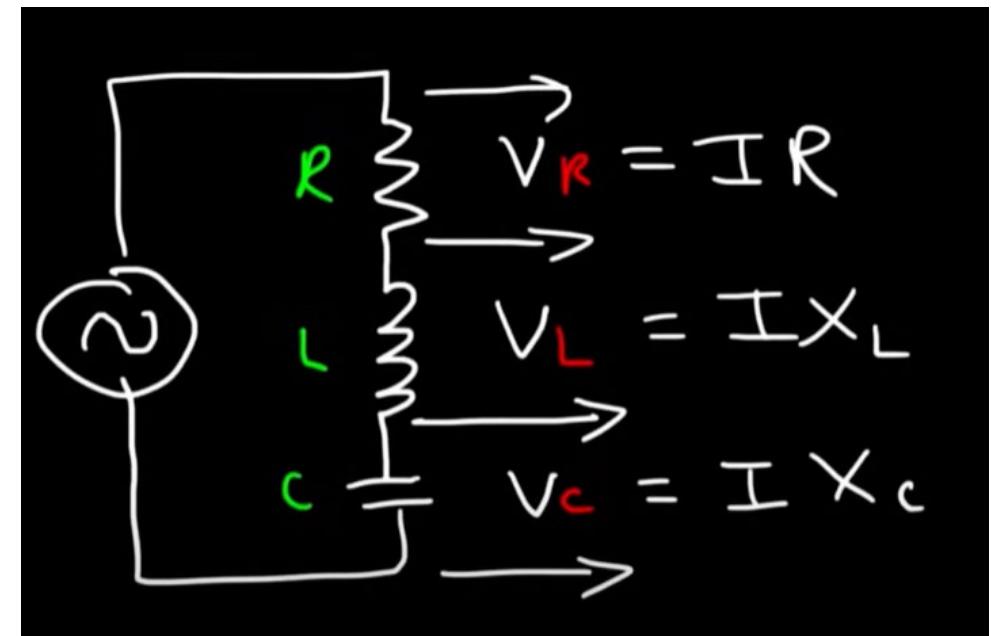
# Series RL, RC and RLC Circuits

---


- We can then work out Voltage or Current for the whole circuit using the equation
  - $V = IZ$
- However, for each component in the circuit we use their individual equation


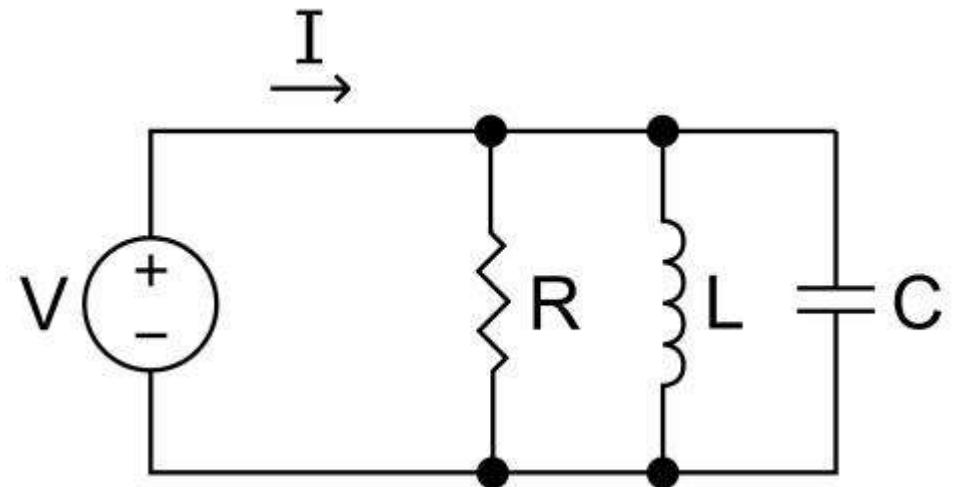
# Parallel RLC Circuits

---


- When we have components in parallel, we work out our impedance differently
- We use the equation:  $Z = \frac{1}{\sqrt{\frac{1}{R} + (\frac{1}{X_L} - \frac{1}{X_C})^2}}$
- Remembering we can sub in 0 if we are missing a capacitor or an inductor


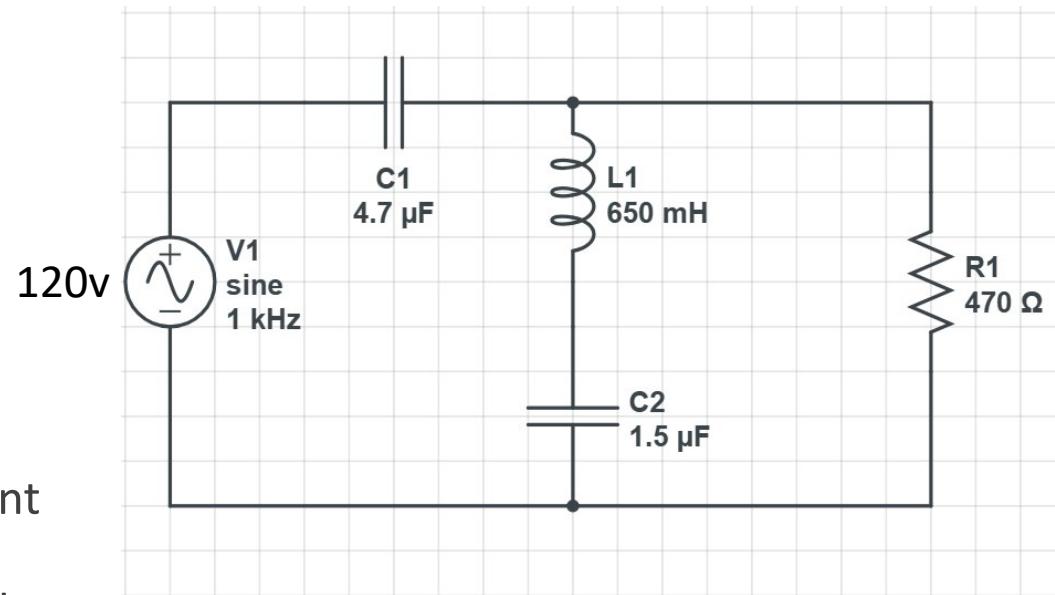
# Example Question

---

- In this question we want to find the voltage and current through every component
- The best strategy to take are to:
  1. Combine components to make equivalent circuits
  2. Continue combining components until the circuit is one equivalent component
  3. Expand circuit back out calculating V and I for the components or groups as we go



# Example Question


---

- Let's start by calculating the reactance for each component

$$\bullet X_{C1} = \frac{1}{2\pi f C} = \frac{1}{2\pi * 1000 * 0.0000047} = 33.86275385$$

$$\bullet X_{C2} = \frac{1}{2\pi f C} = \frac{1}{2\pi * 1000 * 0.0000015} = 106.1032954$$

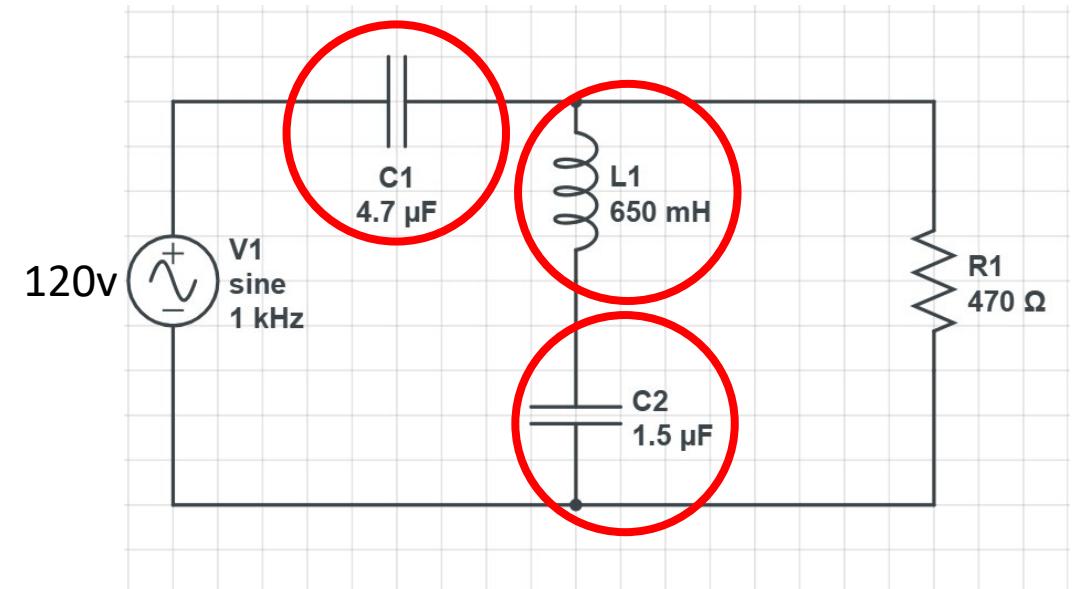
$$\bullet X_{L1} = 2\pi f L = 2\pi * 1000 * 0.65 = 4084.07045$$


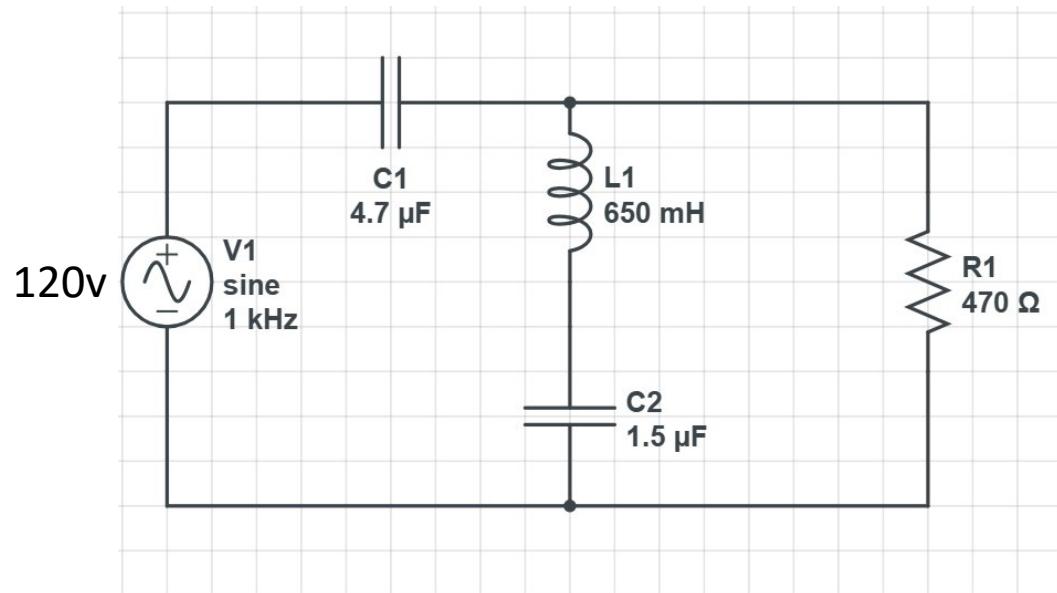
# Example Question

---


- Next let's write out our reactance's as impedances
  - $Z_{C1} = 33.863 \angle -90^\circ$
  - $Z_{C2} = 106.103 \angle -90^\circ$
  - $Z_{L1} = 4084.070 \angle 90^\circ$
  - $Z_{R1} = 470 \angle 0^\circ$


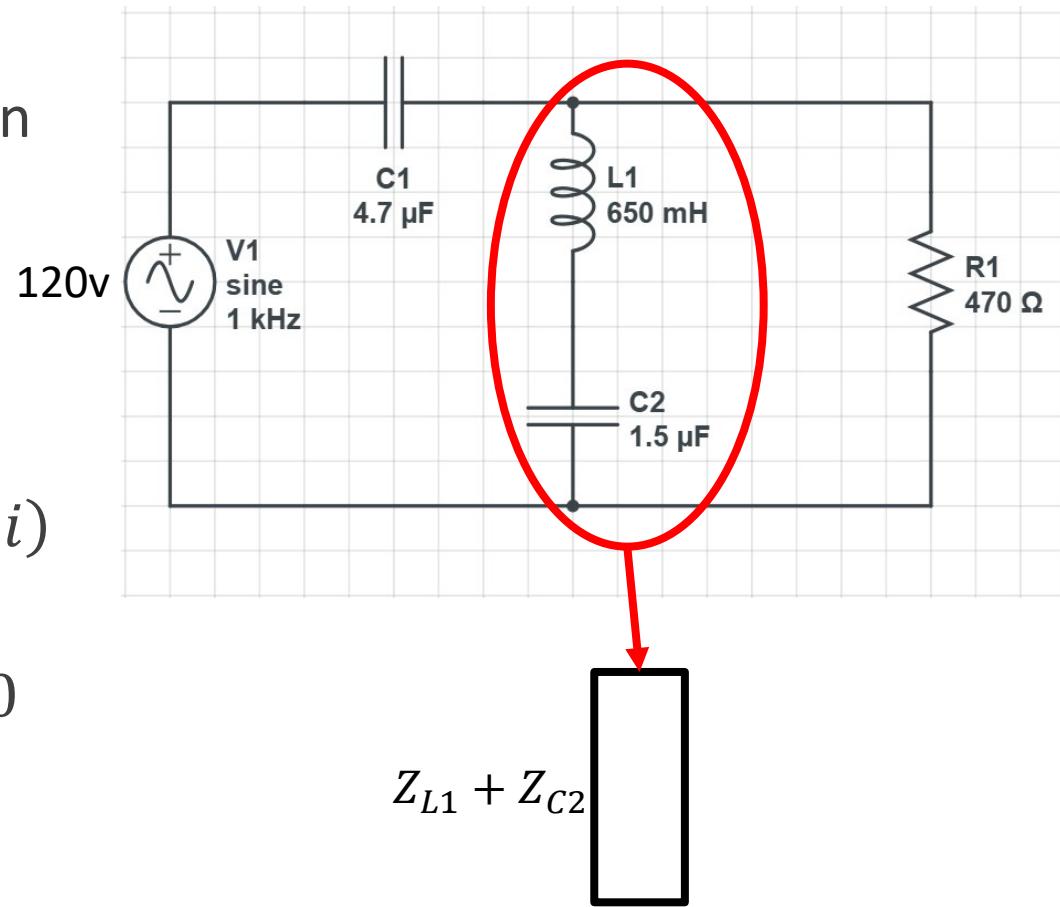
# Example Question

---


- Next let's combine L1 and C2 into an equivalent component
- $Z_{L1} + Z_{C2}$
- $(0 + 4084.070i) + (0 - 106.103i)$
- $(0 + 3,977.967i) = 3977.967\angle90$


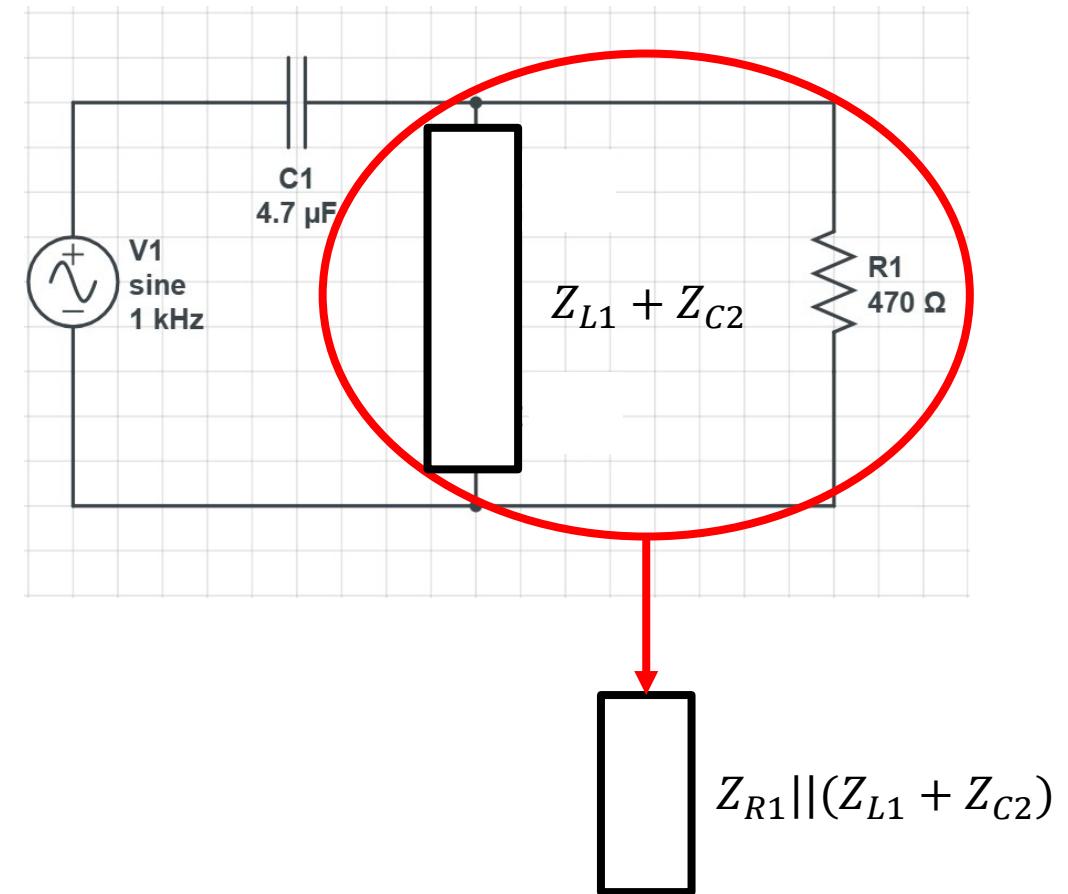
# Example Question

---


- Next let's combine  $R_1$  with our equivalent component
- $Z_{R1} \parallel (Z_{L1} + Z_{C2})$
- $$\frac{1}{\left(\frac{1}{470\angle 0} + \frac{1}{3977.967\angle 90}\right)}$$
- $$\frac{1}{(0.002127659574\angle 0 + 0.00025138469\angle 90)}$$


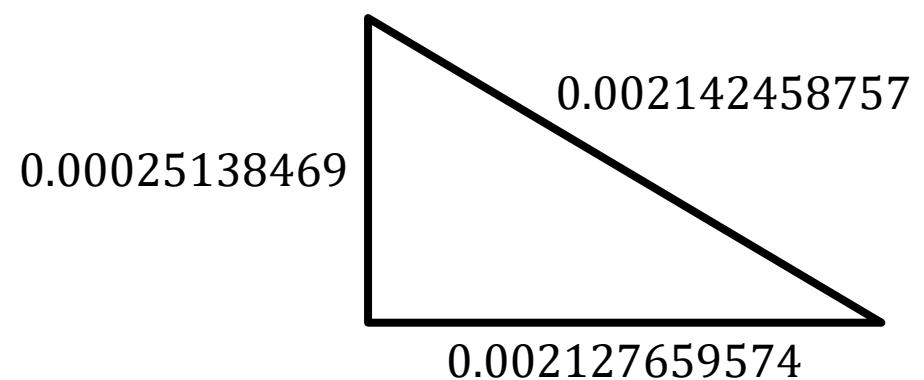
# Example Question

---


- $$\frac{1}{(0.002127659574\angle 0 + 0.00025138469\angle 90)}$$
- $$\sqrt{0.002127659574^2 + 0.00025138469^2}$$
- $$\frac{1}{0.002142458757} = 466.7534424$$
- $$\tan\left(\frac{0.00025138469}{0.002127659574}\right) = 0.1187036715$$
- $$466.7534424\angle 0.1187036715$$


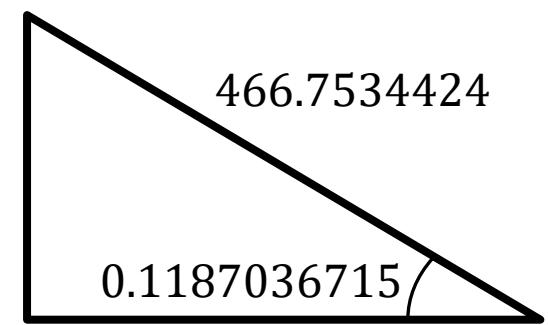
# Example Question

---

- $466.7534424 \angle 0.1187036715$
- Let's convert this back to rectangular form
- $466.7534424 * \sin(0.1187036715) = 55.27532353i$
- $466.7534424 * \cos(0.1187036715) = 463.4688928$
- $(463.4688928 + 55.27532353i)$




$$s_h^o c_h^a t_a^o$$
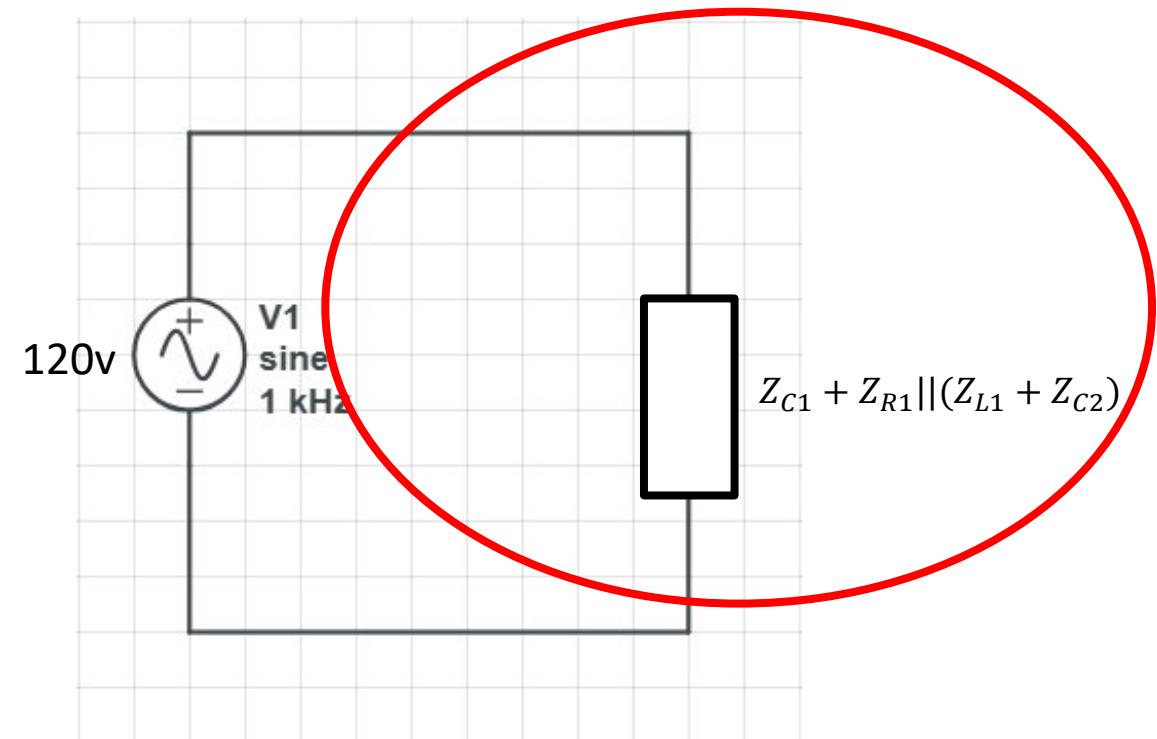
# Example Question

---

- Let's combine our final two components into an equivalent component
- $Z_T = Z_{C1} + Z_{R1} \parallel (Z_{L1} + Z_{C2})$
- $(0 + 33.86275385i) + (463.4688928 + 55.27532353i)$
- $(463.4688928 + 89.13807738i)$
- $\sqrt{463.4688928^2 + 89.13807738^2} = 471.9629344$
- $\tan\left(\frac{89.13807738}{463.4688928}\right) = 0.1947351008$
- $471.9629344 \angle 0.1947351008$



# Example Question

---

- Let's work out the current going through this combined component
- $V = IZ$
- $I = \frac{V}{Z}$
- $I = \frac{120\angle 0}{471.9629344\angle 0.1947351008} = 0.25425725465$

